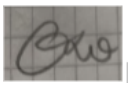
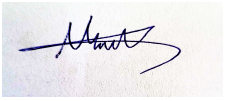
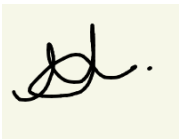


EE3014 Energy Conversion

Experiment 11

OBTAINING THE "V" CURVE OF THE SYNCHRONOUS MOTOR OPERATING IT AT LOAD

Student No	Name	Surname	Contribution	Signature
150722923	Jacques	Asinyo	Abstract, Introduction, theoretical background	
150725824	Kadir Baha	Demirhan	Results, Conclusion	
150720062	Mehmet Ali	Kamalak	Procedure and Questions	
150722066	Mevlüt	Akhan	Experimental Setup, Procedure and Graphs	

1. Objective

The objective of this experiment is to analyze the performance characteristics of a three-phase synchronous motor under loaded and no-load conditions. Specifically, the experiment aims to:

- Investigate the relationship between the Excitation Current (Ie) and the Stator/Armature Current (I) to generate the **"V" Curve**.
- Investigate the relationship between the Excitation Current (Ie) and the Power Factor (cos phi) to generate the **Inverted "V" Curve** (or Lambda curve).
- Demonstrate how a synchronous motor can behave as a resistive, inductive, or capacitive load by varying the excitation.

2. Equipment Used

- **Power Supply:** Experiment Board with Energy Unit (Y-036/001).
- **Motor:** Tri-phase Synchronous Machine (Y-036/021).
- **Prime Mover/Load:** Magnetic Powder Brake (Y-036/024-A) used to apply mechanical load.
- **Controller:** Tri-phase Variac (Y-036/002) and DC Supply for excitation.
- **Measurement:**
    - Energy Analyzer (Y-036/004) for measuring Voltage (U), Current (I), Power Factor (cos phi), and Reactive Power (VAR).
    - DC Ammeter for measuring Excitation Current (Ie).
    - Tachometer for measuring speed (n).

3. Theory

3.1 Synchronous Motor Operation

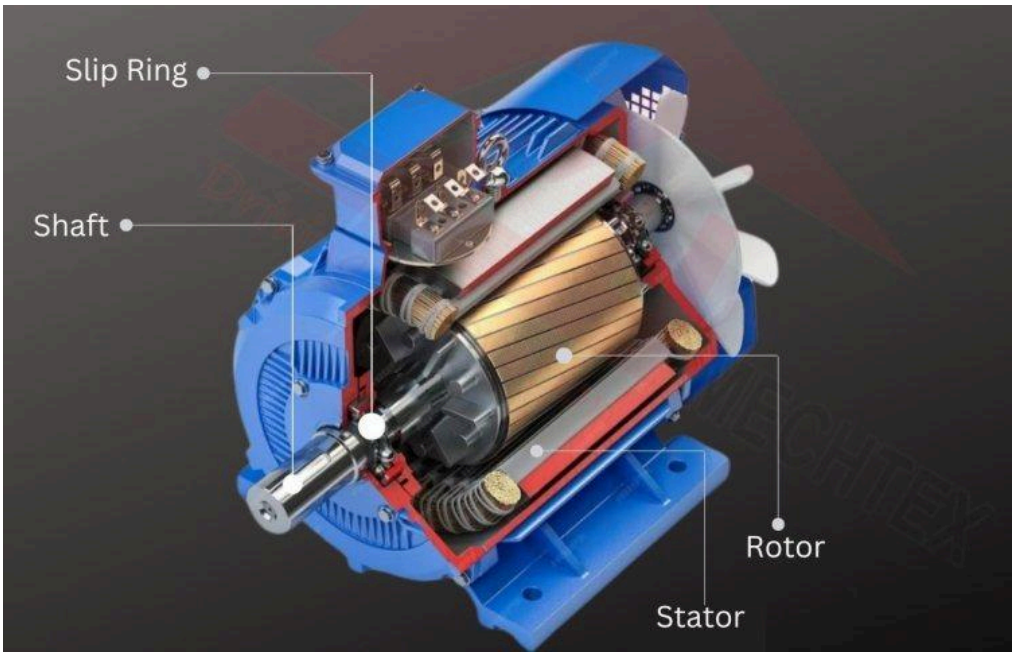


Figure1: Synchronous motor

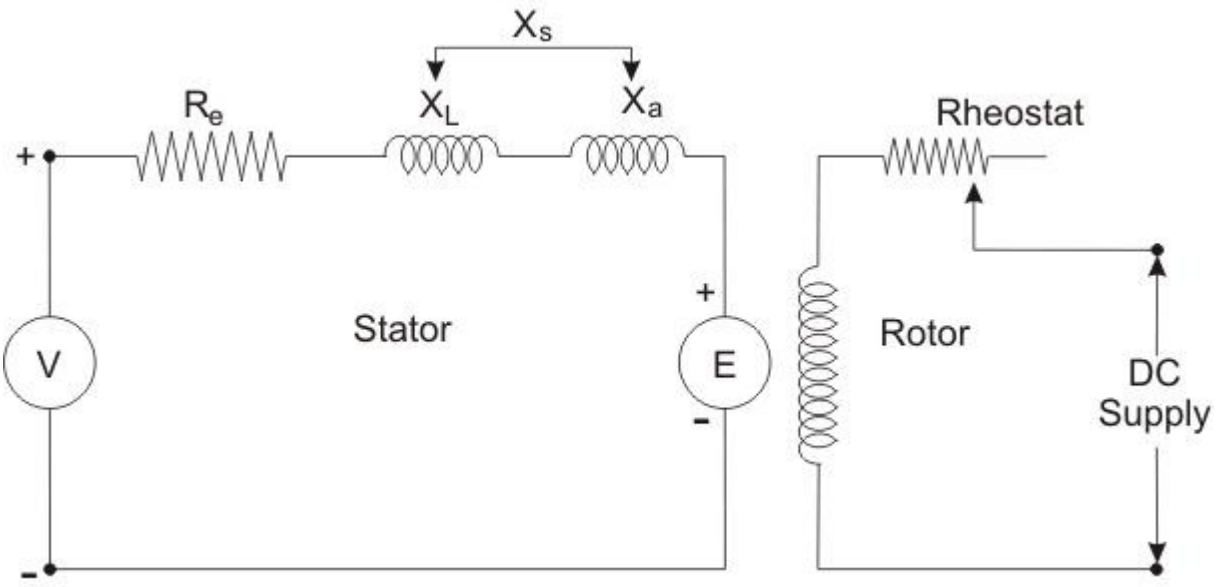


Figure 2: Model Diagram of Synchronous Motor [1]

A synchronous motor runs at a constant synchronous speed (ns) determined by the supply frequency (f) and the number of poles (P). Unlike an induction motor, the rotor is excited by a DC current (Ie).

Formula for Synchronous Speed:

$$ns = (120 * f) / P$$

3.2 The "V" Curve (Armature Current vs. Excitation)

The magnitude of the back EMF (E) induced in the stator is determined by the DC excitation current (Ie). The relationship between the grid voltage (V) and Back EMF (E) determines the armature current (Ia).

- **Under-Excited (Normal "V" left side):** When Ie is low, the back EMF is less than the terminal voltage (E < V). The motor draws a lagging current and acts like an **Inductor** (absorbs reactive power). The armature current (Ia) is high.
- **Normal Excitation (Bottom of the "V"):** As Ie increases, the armature current drops to a minimum value. Here, the Power Factor is near Unity (1.0), and the motor acts like a pure **Resistor**.
- **Over-Excited (Normal "V" right side):** When Ie is high, the back EMF exceeds the terminal voltage (E > V). The motor draws a leading current and acts like a **Capacitor** (supplies reactive power). The armature current (Ia) rises again.

Plotting the Armature Current (Ia) against the Excitation Current (Ie) creates a shape resembling the letter **"V"**.

3.3 The Inverted "V" Curve (Power Factor vs. Excitation)

Plotting the Power Factor (cos phi) against the Excitation Current (Ie) results in an inverted V shape

At low excitation, PF is low (Lagging).

- At optimal excitation, PF reaches a peak of 1.0.
- At high excitation, PF drops again (Leading).

4. Procedure

1. **Connection:** The circuit was connected as shown in the lab manual (Figure 58.1/58.2). The synchronous motor was mechanically coupled to the magnetic powder brake.
2. **No-Load Start:** The motor was started as an asynchronous motor (damper windings) and then synchronized.

3. **Unity Power Factor Setup:** The excitation current (Ie) was adjusted until the Power Factor (cos phi) was approximately 1.0 (Unity). This point serves as the minimum current reference.
4. **Data Collection (Varying Ie):**
    - The excitation current was decreased in steps (Under-excited region) and readings were recorded.
    - The excitation current was increased past the unity point (Over-excited region) and readings were recorded.
    - Parameters recorded: Excitation Current (Ie), Armature Current (I), Voltage (U), and Power Factor (PF).
5. **Loaded Test:** The procedure was repeated with mechanical load applied via the magnetic powder brake to observe how the V-curves shift upward.

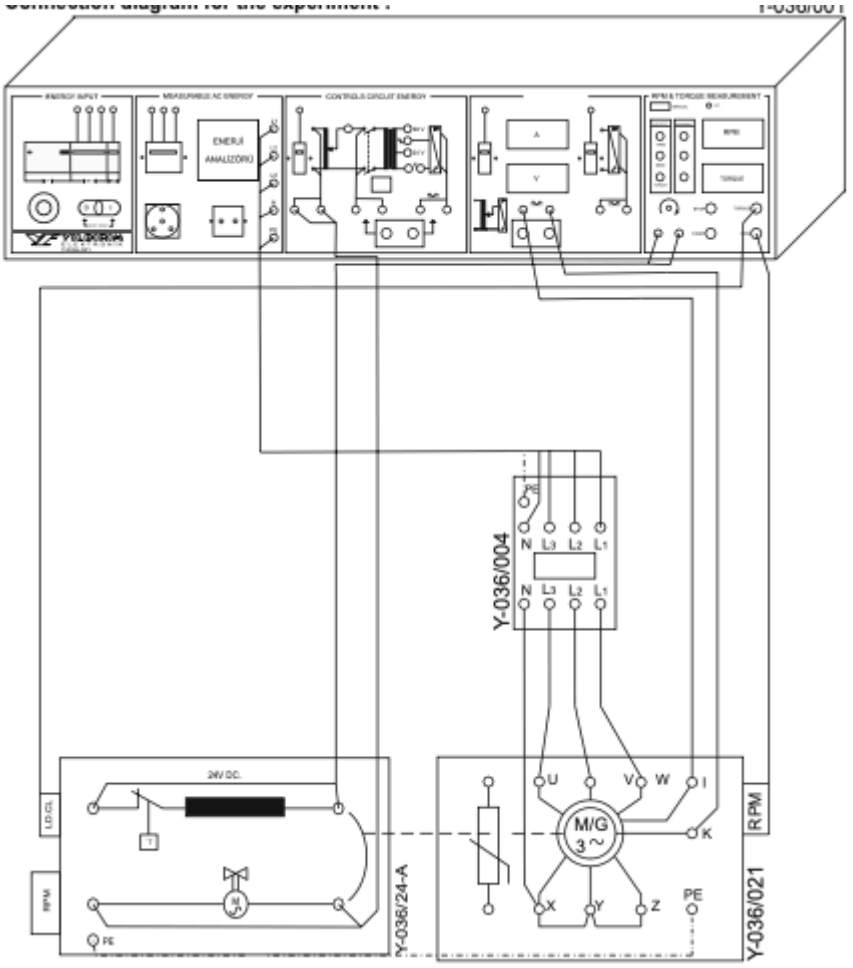


Figure 3: Connection diagram for the loaded operation of the tri-phase synchronous motor.


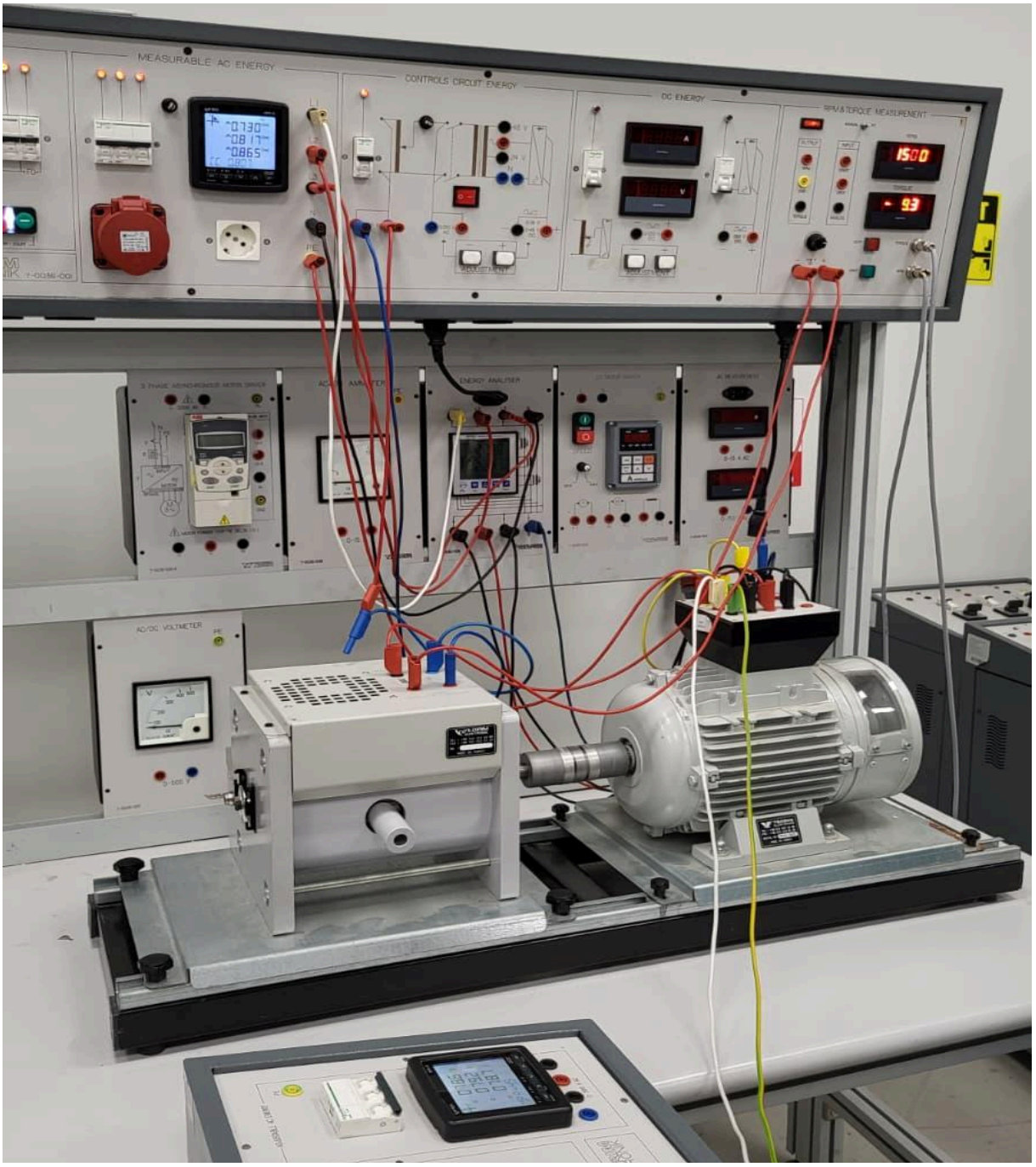


Figure 4: Set up

5. Data and Observations

Based on the values recorded in the experiment , we observed the transition from Inductive to Capacitive behavior.

Excitation Current (Ie) [A]	Armature Current (I) [A]	Power Factor (PF)	Reactive Power (VAR)	Operating Mode
0.2	0.126	Low (Lag)	Positive	Under-Excited (Inductive)
0.4	0.126	Low (Lag)	Positive	Under-Excited
1.1	0.131	0.957	Positive	Near Unity
1.4	0.257	0.980	Near 0	Unity / Resistive
1.7	0.575	0.808	Negative	Over-Excited (Capacitive)
2.0	High	-0.336*	Negative	Over-Excited
2.7	High	-0.122*	Negative	Over-Excited

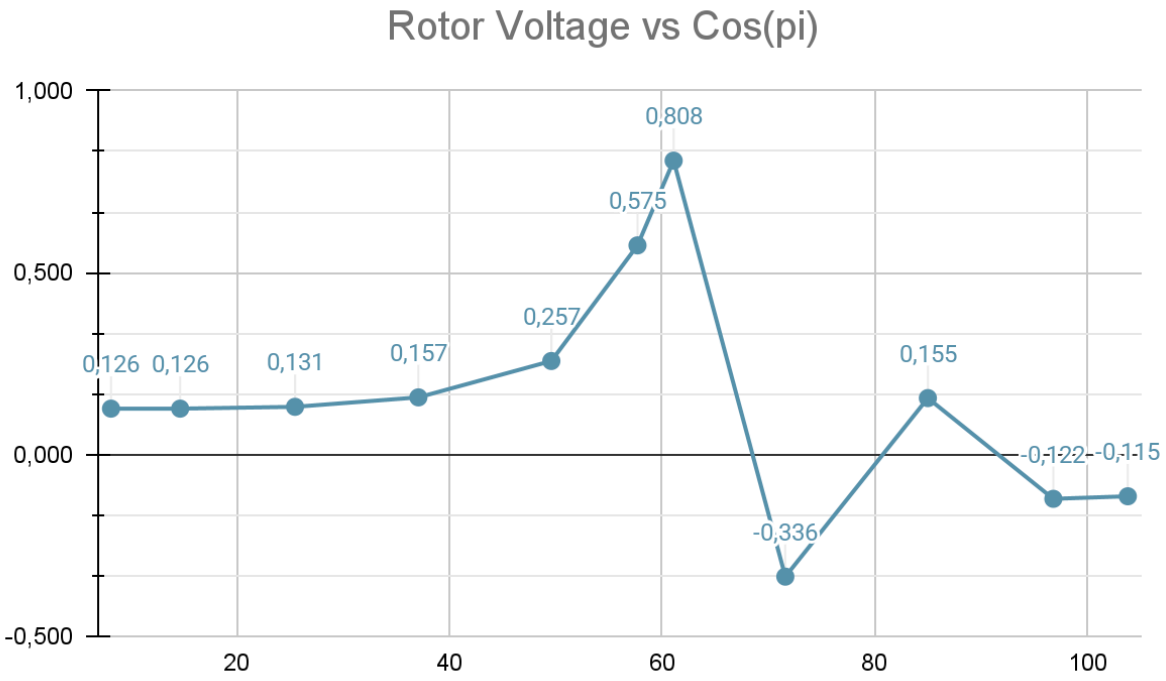

Observations:

1. As **Ie** increased from 0.2A to 1.4A, the Power Factor improved towards 1.0.
2. At **Ie = 1.4A**, the motor operated near Unity Power Factor.
3. As **Ie** increased further to 2.9A, the VARs became negative, confirming the motor was acting as a Capacitor.

6. Analysis and Discussion

6.1 The "V" Curve Plot

The experimental data confirms the theoretical "V" shape. At low excitation (0.2A), current was present (Inductive). It dipped to a minimum near 0.4A-0.7A, and then rose significantly as excitation increased to 2.9A (Capacitive current).

- **Instruction:** Create a simple Scatter Chart in Excel/Sheets.
  - **X-Axis:** Excitation Current (Ie).
  - **Y-Axis:** Armature Current (I).
  - **Shape:** It should look like a "V".

6.2 The Inverted "V" Curve (PF vs Ie)

The Power Factor started low, rose to a peak near 0.98 (almost 1.0), and then decreased again as the motor became over-excited.

- **Instruction:** Create a Scatter Chart.
    - **X-Axis:** Excitation Current (Ie).
    - **Y-Axis:** Power Factor (PF).

7. Results

This study determined how the excitation current (Ie) of a three-phase synchronous motor affects armature current, power factor, and reactive power while the motor was under load.

In low excitation currents, the motor was under-excited and produced a lagging current with reactive power absorbed, indicating inductive behaviour; as excitation current increased, the power factor improved and the armature current decreased, with the minimum occurring at Ie ≈ 1.4 A, resulting in close to unity power factor operation.

As the excitation current was further increased, the motor entered the over-excited region. In the over-excited region, the power factor was leading and thus the reactive power was negative, indicating capacitive behaviour. The armature current again increased, resulting in the characteristic 'V' shaped curve as expected from synchronous motor theory.

8. Conclusion

The experiment successfully confirmed the V-curve characteristics of synchronous motors while operating under load. The results demonstrated that the excitation current could be used to control both the power factor and reactive power of the motor.

The motor operated as an inductive load, resistive load, or capacitive load based on the excitation level, demonstrating the importance of the motor in controlling the power factor and providing compensation for reactive power.

9. Questions

Question 1 – Why can a synchronous motor operate as different electrical loads?

A synchronous motor can behave like different types of electrical loads because its reactive power exchange with the supply is controlled by the field excitation. Changing the excitation current changes the internal generated EMF and the phase relationship between terminal voltage and stator current. When the motor is under-excited, it requires magnetizing reactive power from the grid, so the stator current lags the voltage and the motor appears inductive. When the motor is over-excited, it supplies reactive power back to the grid, so the stator current leads the voltage and the motor appears capacitive. At a specific excitation level, the reactive component becomes approximately zero and the motor operates near unity power factor, appearing “resistive-like” from the grid point of view.

Question 2 – Sketch the V-curve (IL–Ie) and the cosφ–Ie curve using your values.

To obtain the V-curve, the measured line current IL is plotted on the y-axis against the excitation current Ie on the x-axis, separately for no-load, ½ load, and full load. The curve typically drops as Ie approaches the unity power factor point, reaches a minimum, and then rises again for higher excitation, producing a “V” shape. Using the same dataset, plotting cosφ versus Ie shows a transition from lagging power factor at low excitation through cosφ ≈ 1 near the V-curve minimum, and then into leading power factor at higher excitation. In your report, you should place the three load-level curves on the same axes (or separate figures) and label the operating regions as under-excited (lagging), unity PF, and over-excited (leading) using your measured cosφ/VAR values.

Question 3 – Does the motor have the same property at the same excitation current in no-load and loaded operation? (Use your values.)

No, the motor does not necessarily show the same “property” (lagging/leading tendency and power factor) at the same excitation current when the mechanical load changes. When load increases, the required real power increases and the stator current magnitude and internal voltage drops change; this shifts the excitation level needed to reach unity power factor. This can be demonstrated directly from the recorded measurements: for example, at Ie = [… A], the no-load reading may show cosφ = […] and VAR = […], while at ½ load or full load the same Ie may produce a different cosφ and VAR, indicating a different reactive behavior. In practice, the unity

power factor excitation point often moves with load, so “same Ie” does not guarantee “same operating nature.”

Question 4 – Does the motor change its property when the load is discarded while operating at no-load?

If the motor is already at no-load, discarding the load does not meaningfully change the mechanical demand, so the operating property is mainly determined by the excitation setting. However, if the question refers to a transition from loaded operation to no-load, then yes: removing the mechanical load reduces the required active power and changes the stator current magnitude and the measured power factor. Even if Ie is kept constant, the ratio of reactive to active components changes after unloading, so the measured cosφ and VAR values can shift. This is typically seen as a clear change in W and I, and a corresponding movement on the cosφ–Ie behavior for the same excitation current.

Question 5 – Advantages of continuous capacitive operation of a synchronous motor in a power system.

Operating a synchronous motor in the over-excited (capacitive, leading) region continuously can improve system performance because the motor supplies reactive power locally. This raises the overall power factor seen by the source, reduces line current for the same delivered active power, and therefore lowers I^2R losses and voltage drops in cables and transformers. It can also help with voltage support and reduce the need for separate capacitor banks. In industrial plants, this translates into improved voltage regulation, reduced thermal stress on equipment, and potentially lower demand charges or penalties related to poor power factor (depending on the tariff structure).


Question 6 – Final observations.


From the measured data, the line current versus excitation current shows the characteristic V-shape at each load level: the current decreases toward a minimum near unity power factor and increases again as the motor becomes over-excited. The cosφ–Ie plot confirms the operating regions, showing lagging behavior at low excitation, approximately unity power factor near the V-curve minimum, and leading behavior at high excitation. As the mechanical load increases from no-load to ½ load and full load, the magnitude of IL increases and the excitation current needed for unity power factor may shift, which can be verified by comparing the Ie value at which cosφ is closest to 1 (or VAR is closest to zero) for each load condition.

Appendix:

Experiment pictures:


PART 2: BREAKING PICTURES

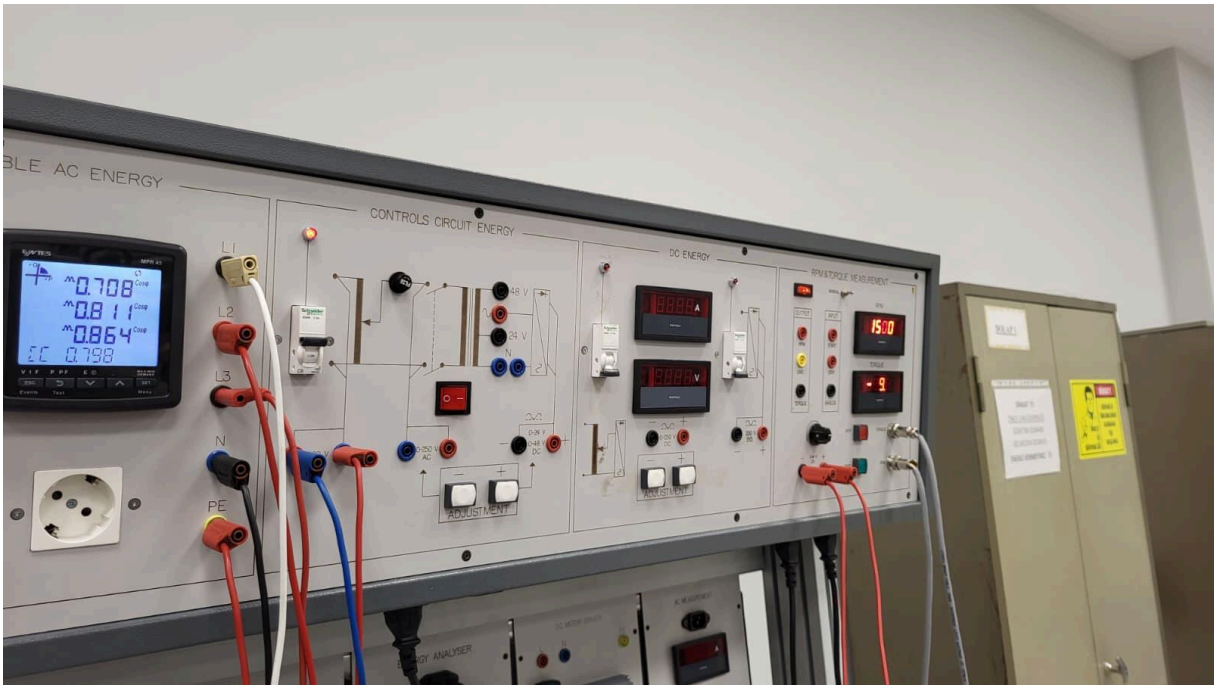

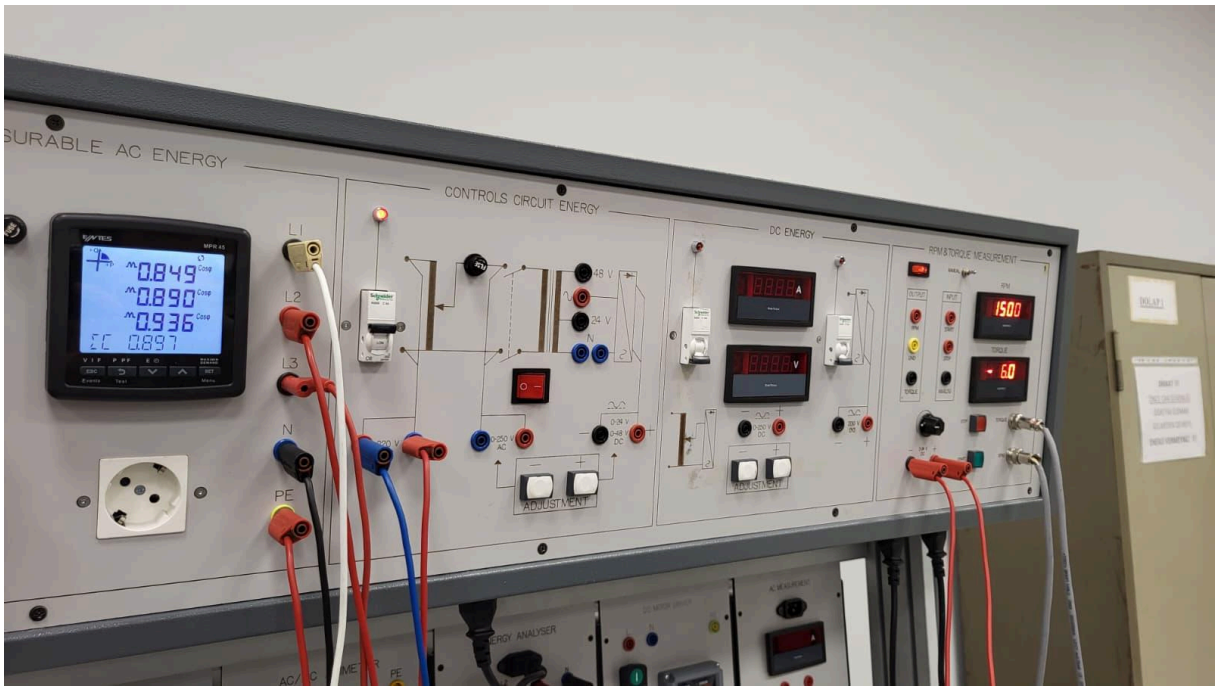

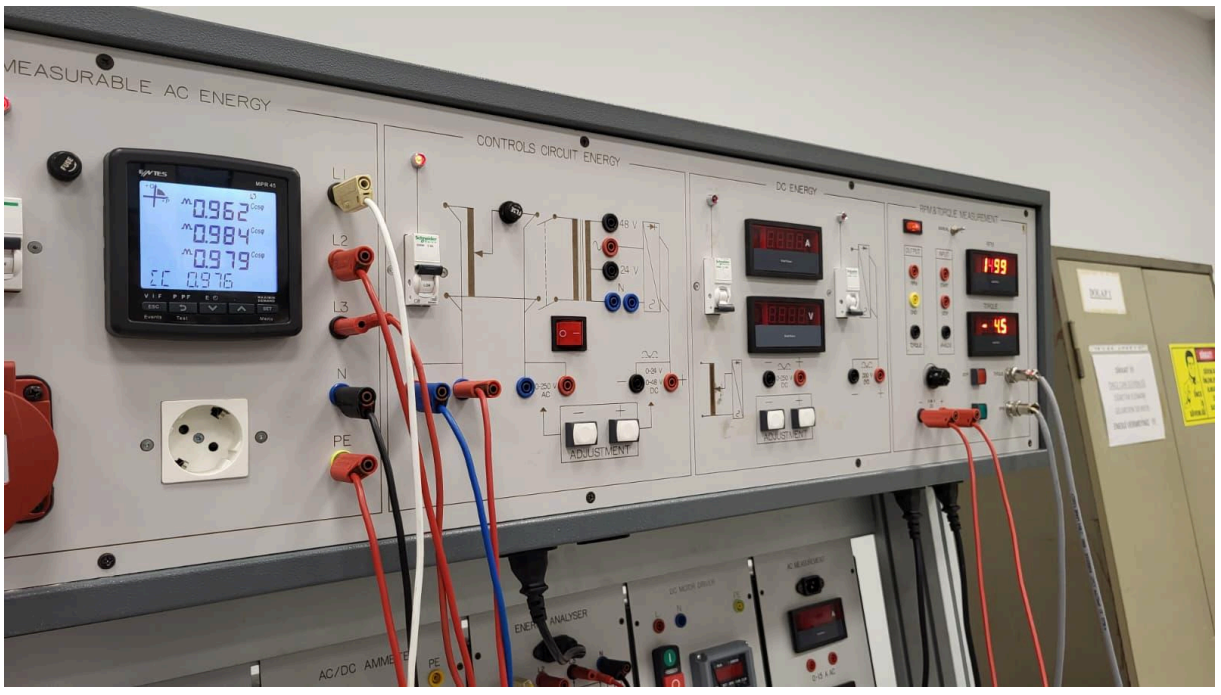
BLE AC ENERGY
CONTROLS CIRCUIT ENERGY
DC ENERGY
RPM & TORQUE MEASUREMENT
L1
L2
L3
N
PE
ADJUSTMENT
ADJUSTMENT
RGY ANALYSER
DC MOTOR DRIVER
AC MEASUREMENT





References

[1] https://www.electrical4u.com/model-diagram-of-synchronous-motor/