
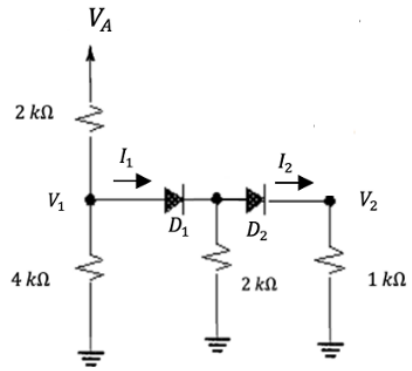
1) Find the values of I_1, I_2, V_1 and V_2 in the circuit below. Use the ideal diode model. Show all steps. Put answers in table.




V_A	V_1	V_2	I_1	I_2

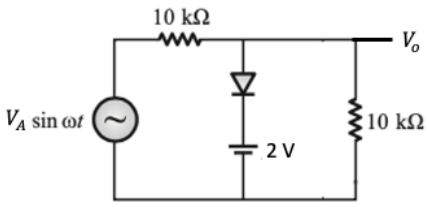2) Use the ideal diode model in the circuit below and find $V_{o(\max)}$ and $V_{o(\min)}$. Show all steps.



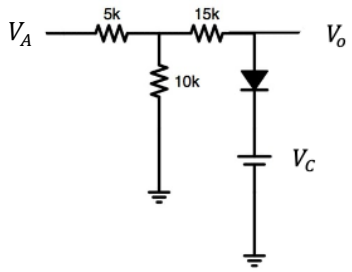3) For the circuit below, find the output V_o for each value of V_C and record in the table. Take $V_{DO} = 0.7\,V$ for the diode. Show all steps.



V_A	V_C	V_o
	-1 V	
	8 V	