
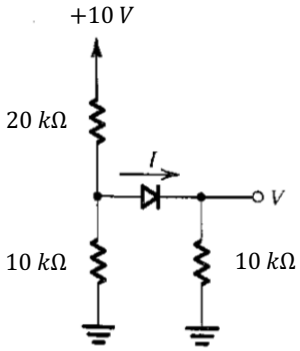
1) Find the value of the indicated current and voltage. $V_{DO} = 0.7\,V$. Show all steps.




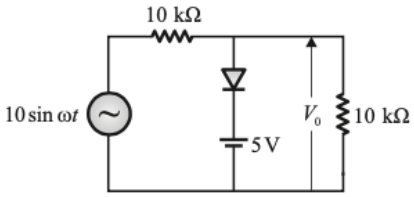
2) For the circuit below, draw the waveform for $V_o$. $V_{DO} = 0.7\,V$.




3) For the circuit below, find the output for each value of the input and record in the table. Use the ideal diode model.

| $V_i$ | $V_o$ |
|---|---|
| -3 V | |
| 0 V | |
| 3 V | |
| 10 V | |

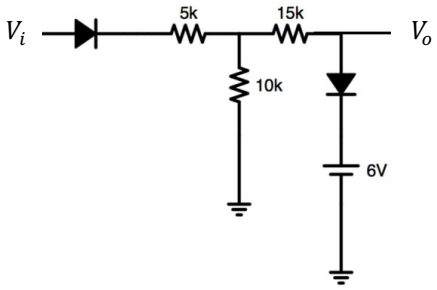


4) Analyze the circuit to find currents in each diode. Use the ideal diode model.

