Freq. Response of Amplifiers Experiment 3

ID & Name:
150720823 – Nurullah Said Tüğmen

Pre-LAB Work

1. For the circuits given in Fig. 1, calculate the low (f_L) and high (f_H) cut-off frequencies. Assume β=200, Cμ=3pF, Cπ=15pF. (Vcc=15V and Vee=-15V)


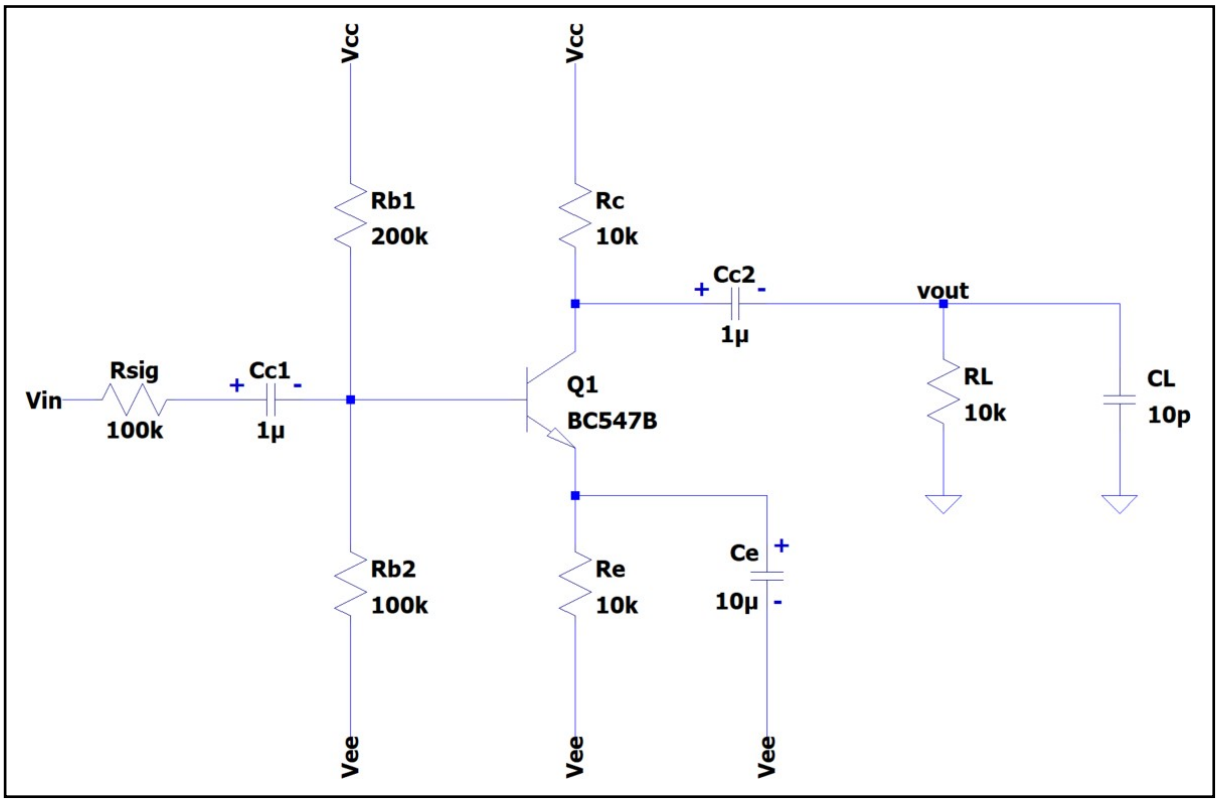


Figure 1

Answer:


Answer: F low = 105,7 (Hz)

F high = 88K (Hz)

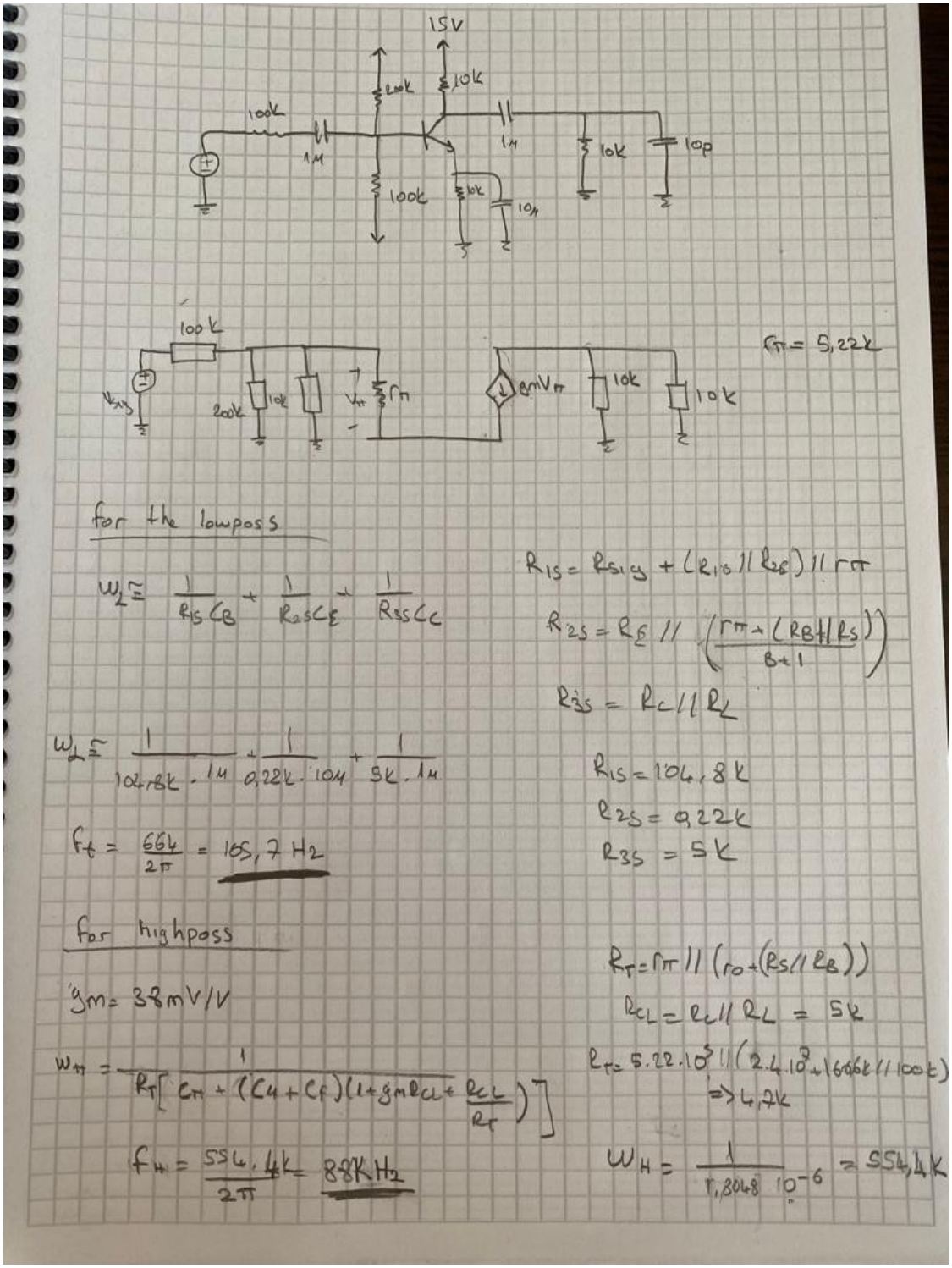

2. Simulate the circuit in Fig. 1 with SPICE. Let Vcc=15V and Vee=-15V. Conduct an AC analysis using the following spice command and plot the amplitude of the frequency response. Indicate the low (f_L) and high (f_H) cut-off frequencies.

   .ac dec 10 1 10e6

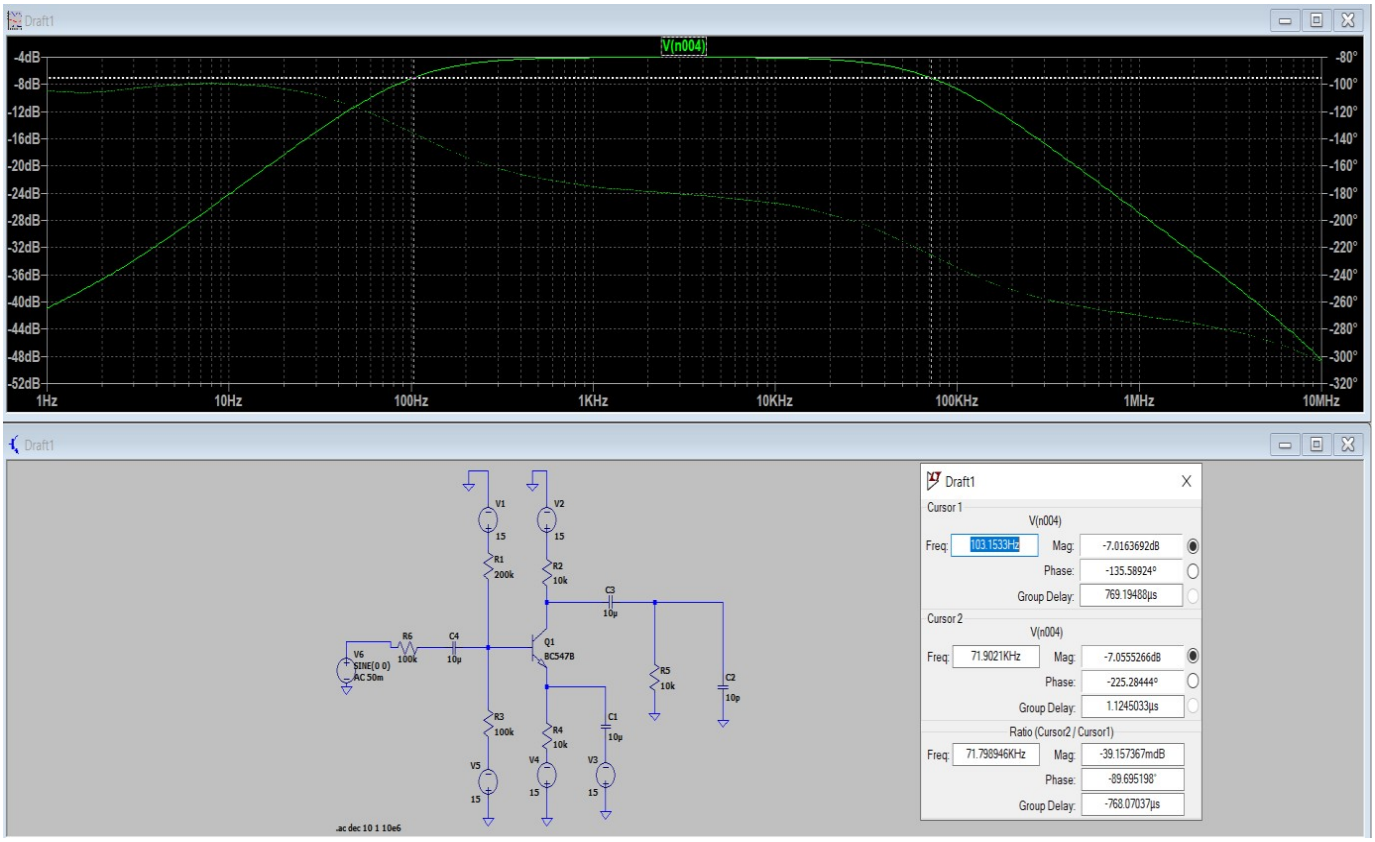

3. For the circuits given in Fig. 2, calculate the low (f_L) and high (f_H) cut-off frequencies. Assume β=200, Cμ=3pF, Cπ=15pF. (Vcc=15V and Vee=-15V)


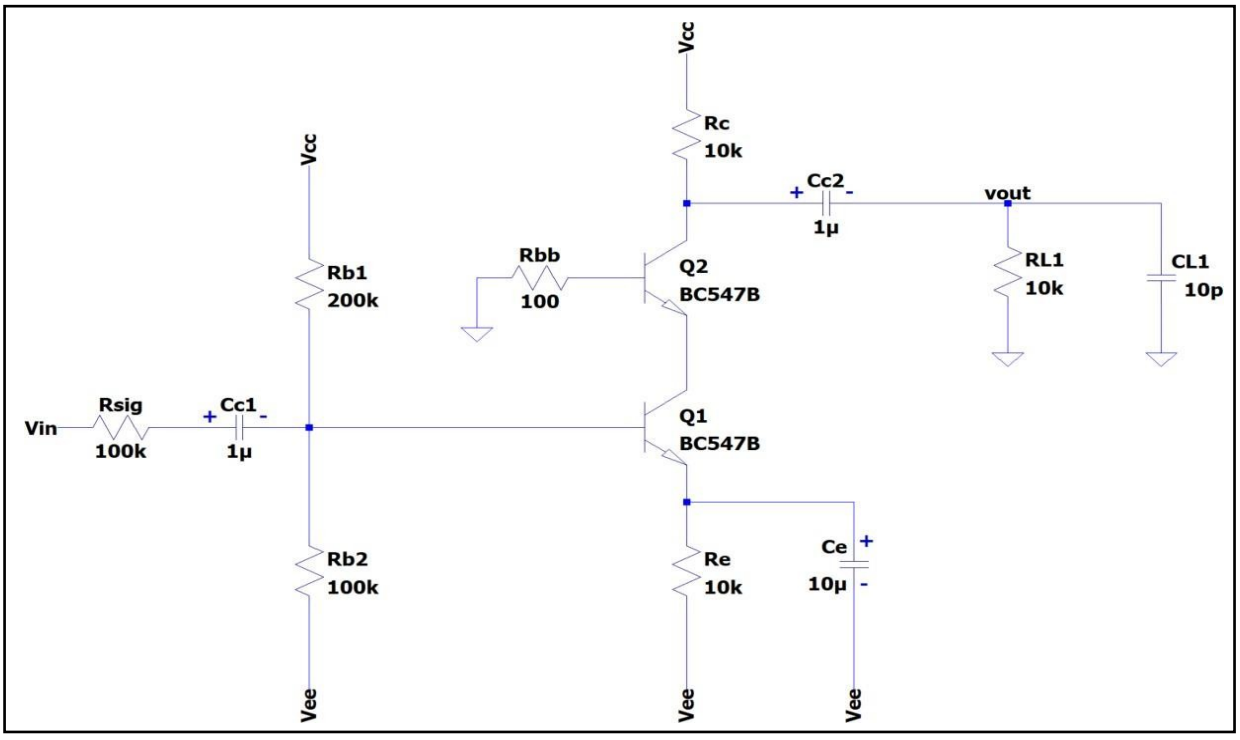



Figure 2


Freq. Response of Amplifiers Experiment 3

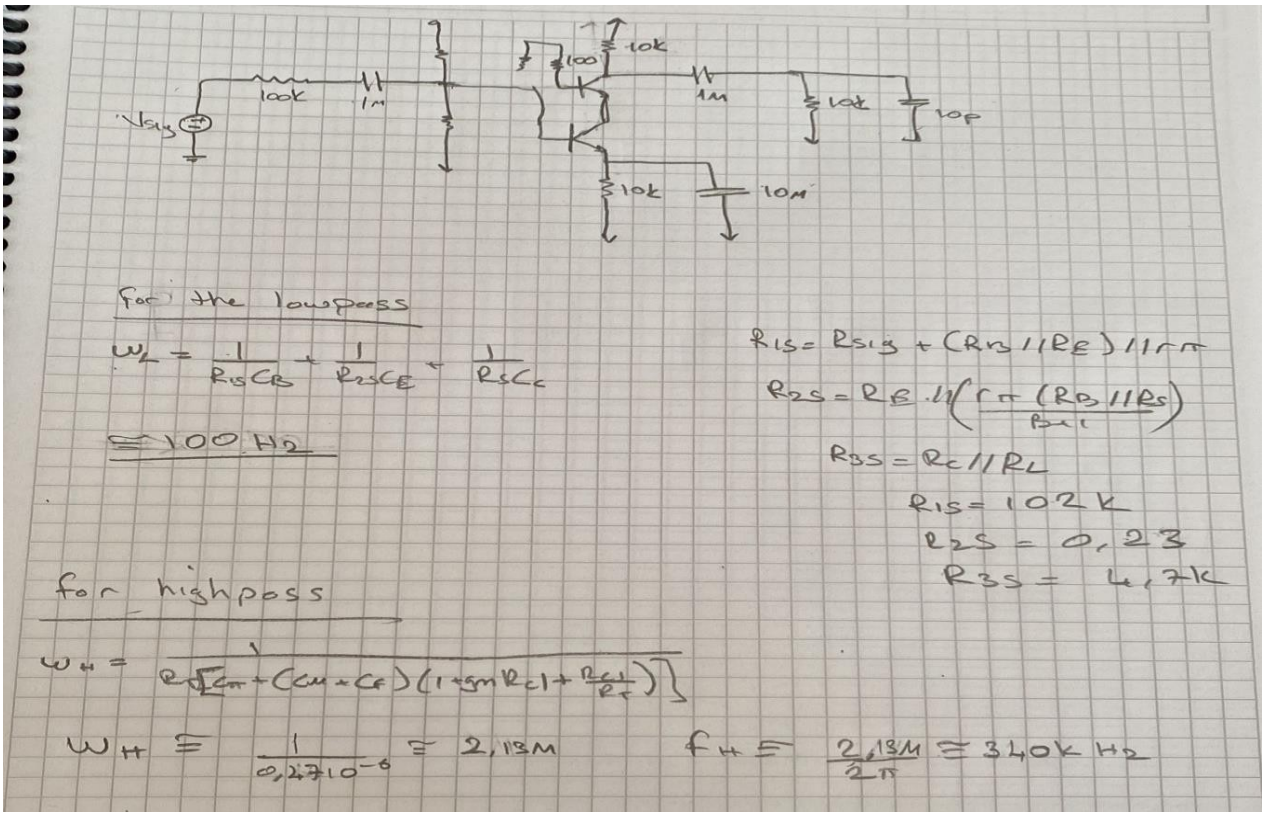Answer: Answer: F low = 100 (Hz)
F high = 340K (Hz)



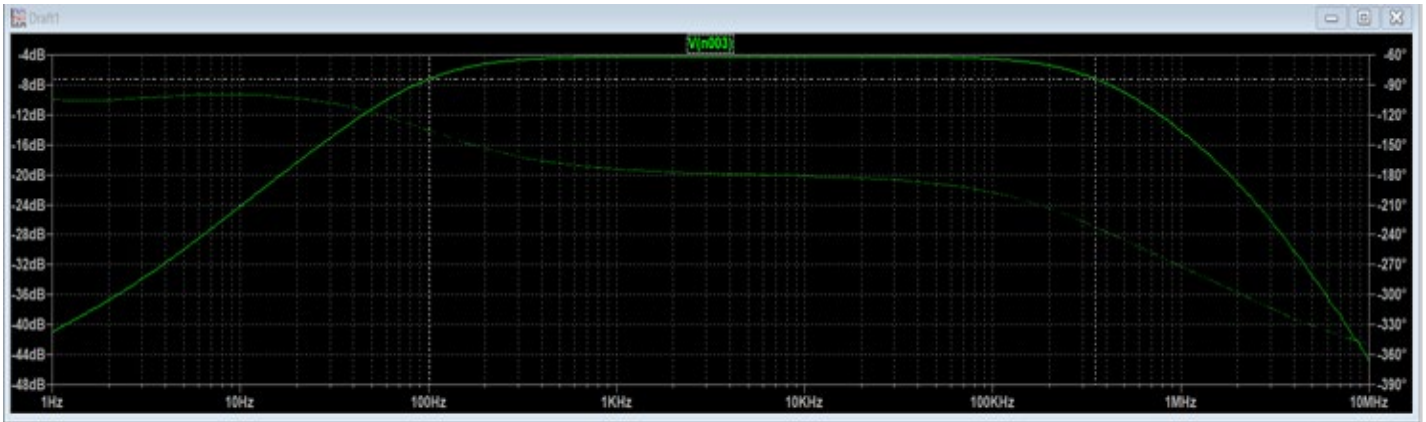4. Simulate the circuit in Fig. 2 with SPICE. Let Vcc=15V and Vee=-15V. Conduct an AC analysis and plot the amplitude of the frequency response. Indicate the low (f_L) and high (f_H) cut-off frequencies.



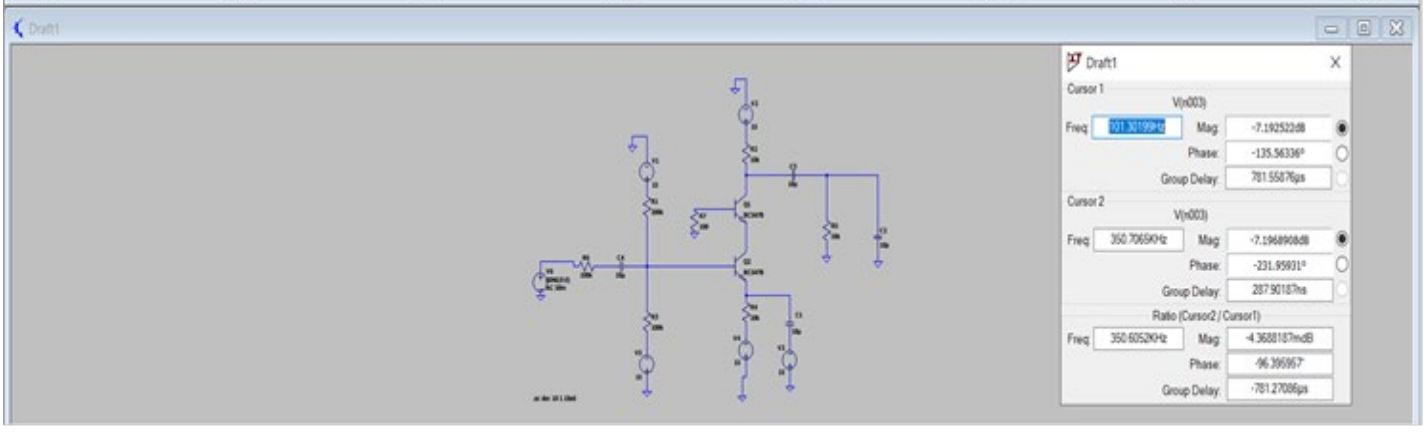

Equipment/Component List


Table 1: Equipment/Component List

Equipment/Component	Model/Value	Count
Breadboard	-	1
Resistor	100Ω	1
Resistor	10kΩ	**3**
Resistor	100kΩ	**2**
Resistor	200kΩ	1
Capacitor	10pF	1
Capacitor	1µF	2
Capacitor	10µF	1
BJT (npn)	BC547	**2**
Multi-meter	-	1
Function Generator	-	1
Oscilloscope	-	1
Voltage Source	15V, -15V	1
Probes & Cables	-	-

Experiment Procedure

5. Adjust Vcc to 15V and Vee to -15V. You will also need the ground connection. Do not connect the supplies.
6. Set-up the circuit in Fig. 1. Be very careful while connecting the capacitor. The +/- pins must be connected as shown in the Fig. 1.
7. Connect the ground and then Vee and Vcc.
8. Apply sine waves of 10Hz, 100Hz, 1kHz, 10kHz, 100kHz, 1MHz, 10MHz with amplitudes of 50mV to Vin.
9. Also find the 3-dB cut-off frequencies.
10. Plot the gain in dB as a function of the frequency. Indicate the low (f_L) and high (f_H) cut-off frequencies.

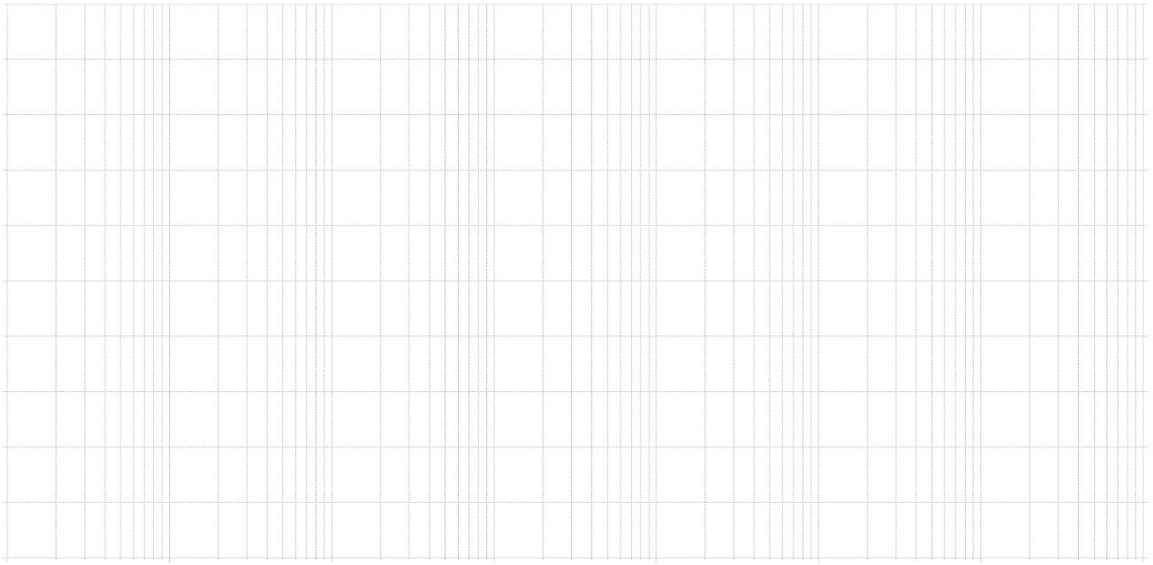11. Power down and disassemble the circuit.
12. Set-up the circuit in Fig. 2. Be very careful while connecting the capacitor. The +/- pins must be connected as shown in the Fig. 2.
13. Connect the ground and then Vee and Vcc. Power up your circuit.
14. Apply sine waves of 10Hz, 100Hz, 1kHz, 10kHz, 100kHz, 1MHz, 10MHz with amplitudes of 50mV to Vin.
15. Also find the 3-dB cut-off frequencies.
16. Plot the gain in dB as a function of the frequency. Indicate the low (f_L) and high (f_H) cut-off frequencies.



17. Compare the calculated (step 1, 3), simulated (step 2, 4) and measured (step 10, 16) responses.

Answer: