

Q1

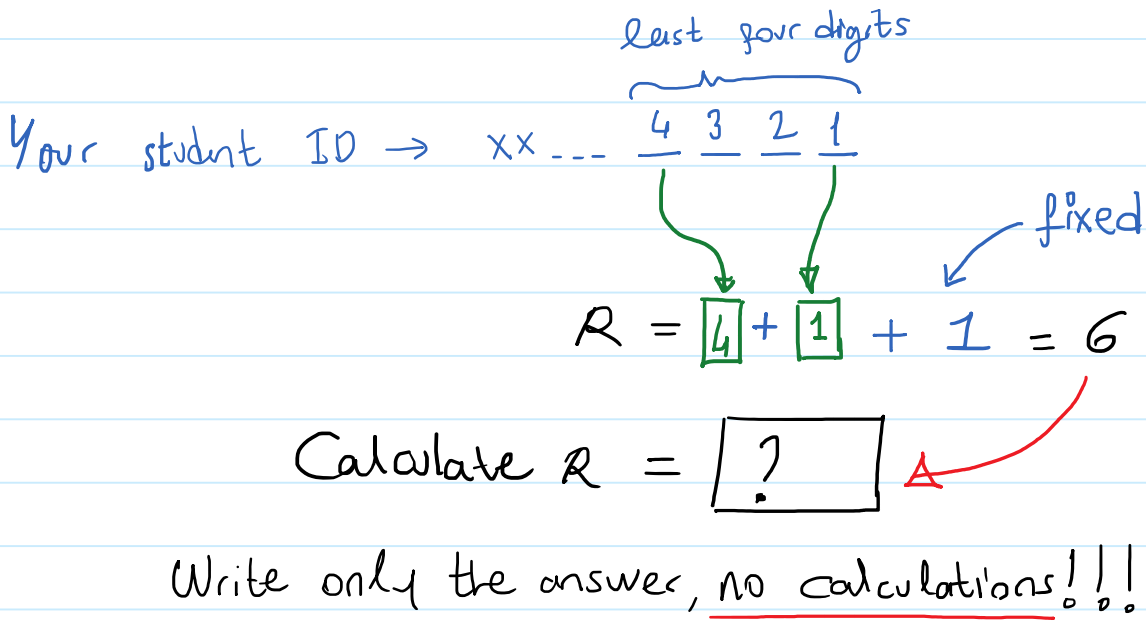

Write only the answer, no calculations!!!

Q2

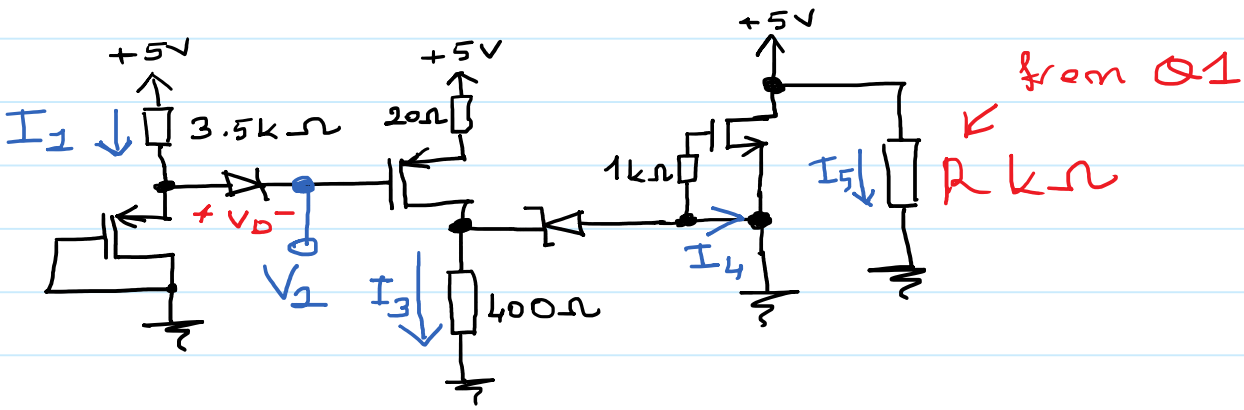

① $V_{tn} = |V_{tp}| = 0.5V$ $\quad k_n = k_p = 2mA/V^2$

② $V_D = 0.7V$ when the diode is forward biased.

③ The zener diode is rated for 2.7V at 2mA current with an incremental resistance of 100Ω.

Find $I_1 = ?$, $V_2 = ?$, $I_3 = ?$, $I_4 = ?$, $I_5 = ?$