Group no: 2.3


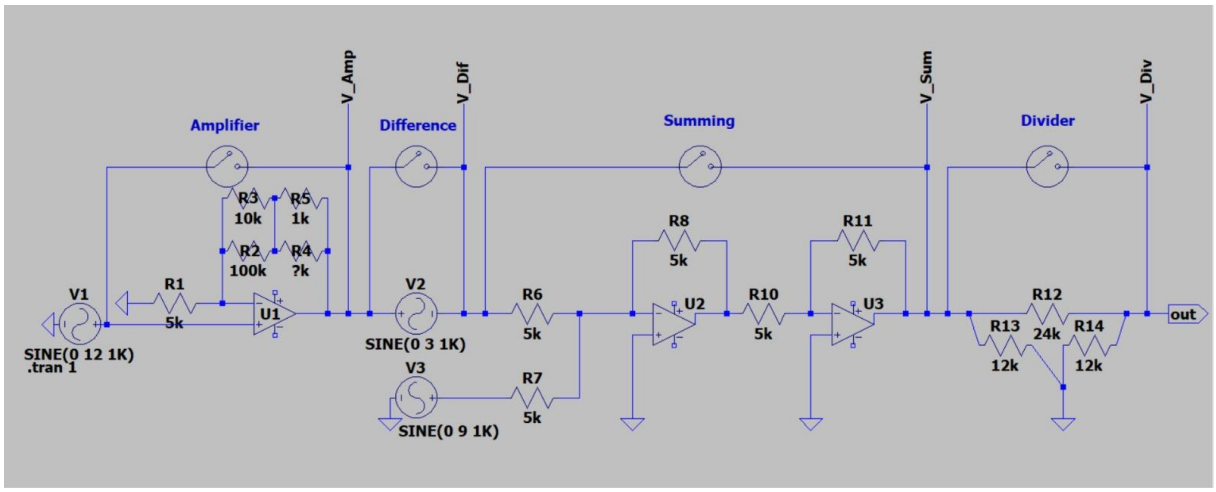



Figure 1:circuit

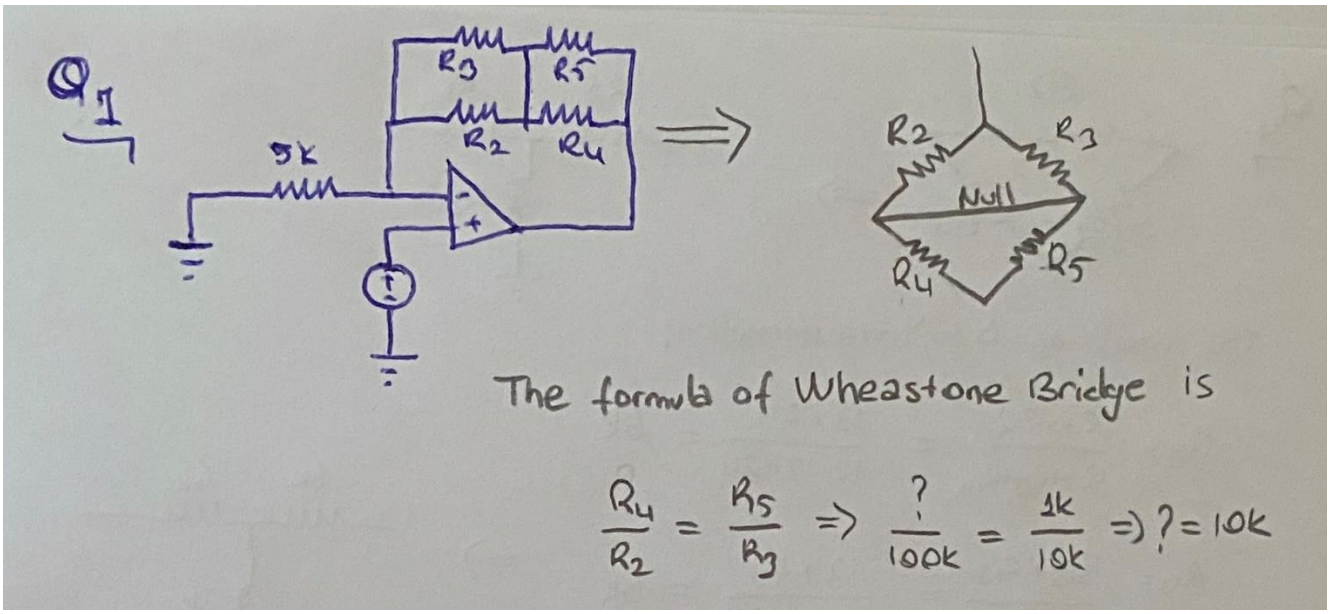
1.Firstly, in the Amplifier section, there is a Wheatstone bridge structure. Using this, find the missing value of R4.



Group no: 2.3

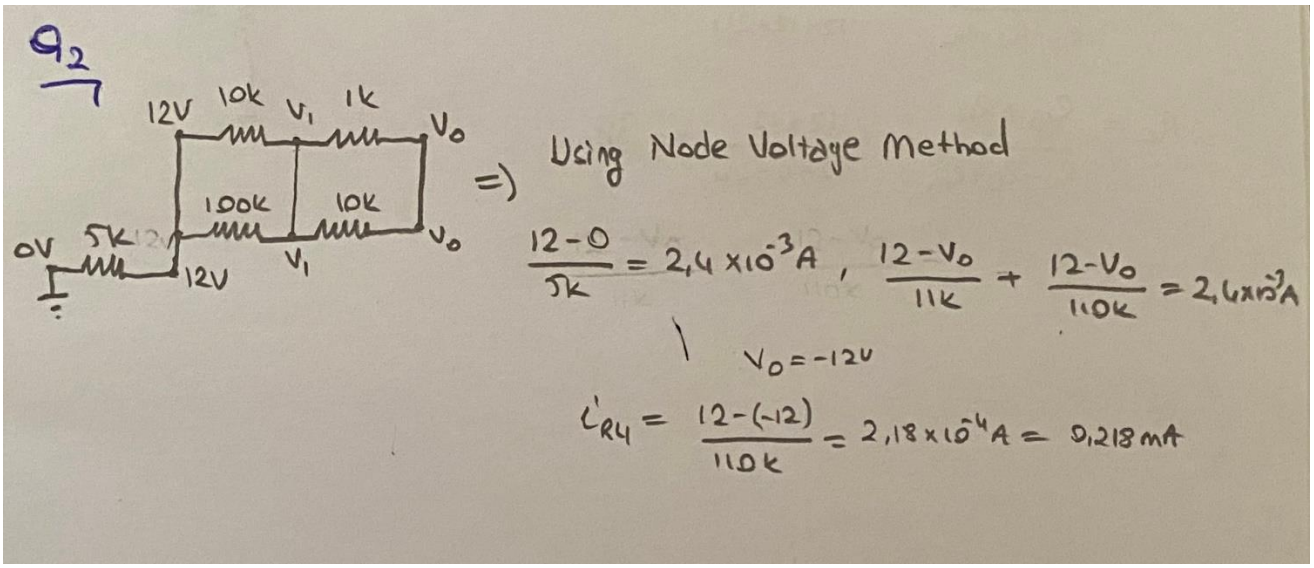
2. After finding R4 value find the current flowing through R2.3.



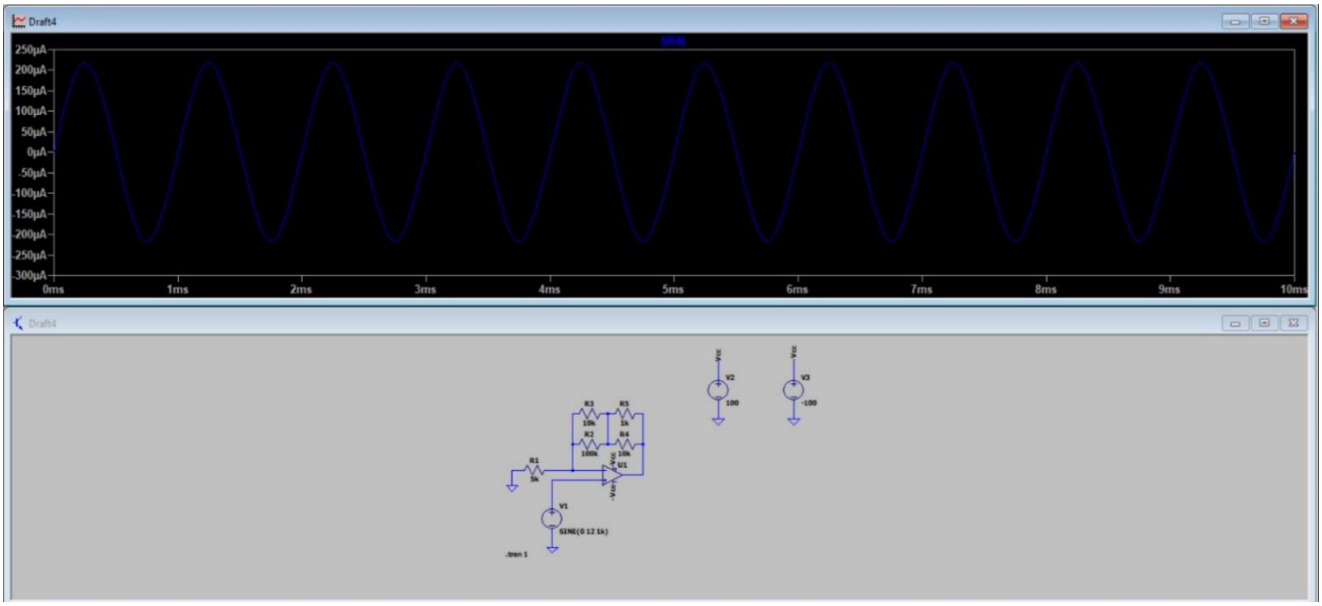

Group no: 2.3

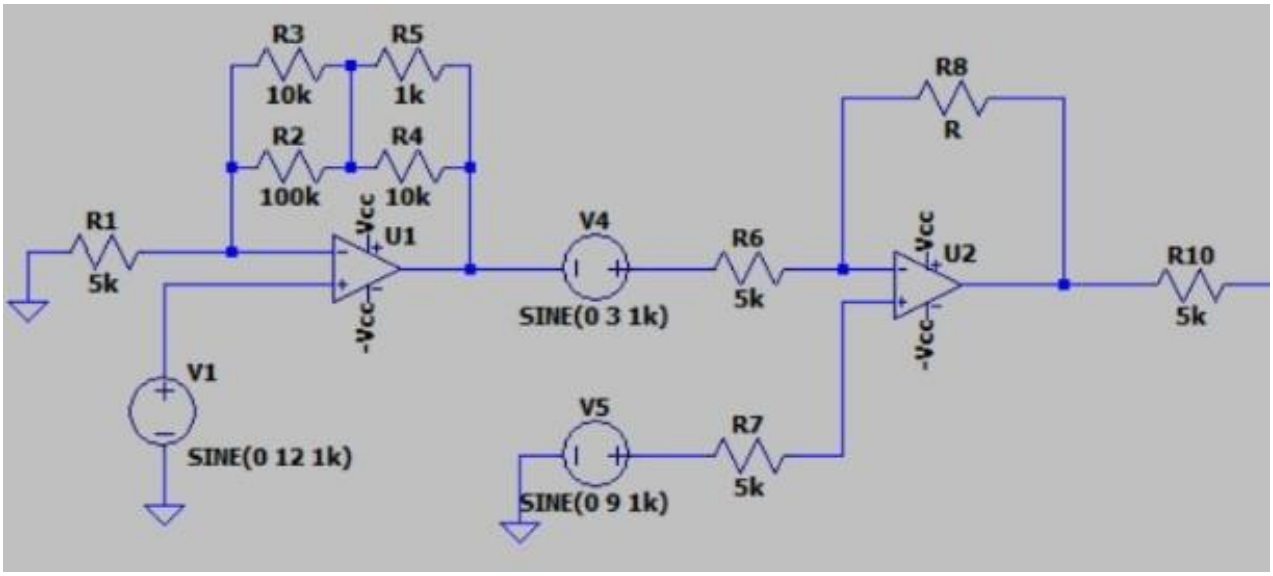
3. Afterward, in the Summing section, there is a second op-amp that inverts the negative output of the first one. Investigate ways to simplify the circuit while still obtaining a positive result and draw the final form of the circuit.




We use a Non-Inverting Operational Amplifier instead of two Inverting Amplifier not to change the voltage polarity.

Group no: 2.3

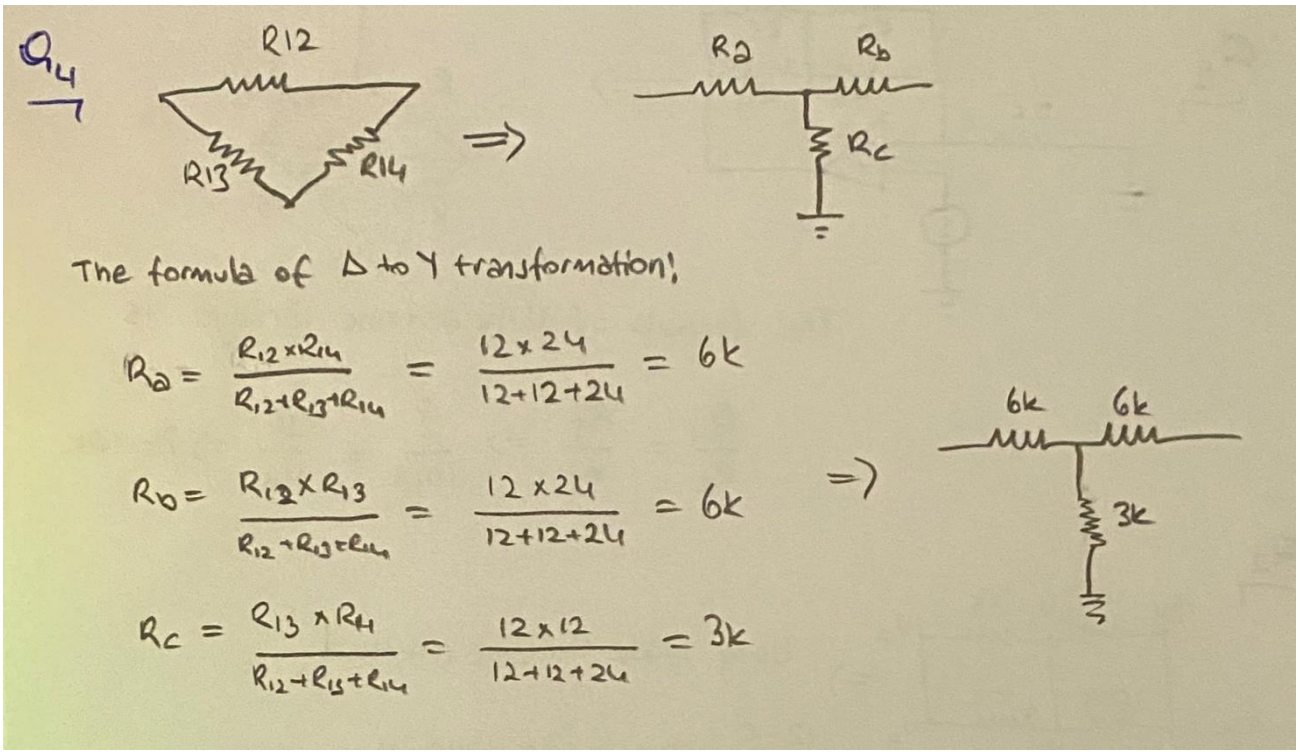
4. Apply delta-wye transformation to the divider part, then apply the changes to the circuit.



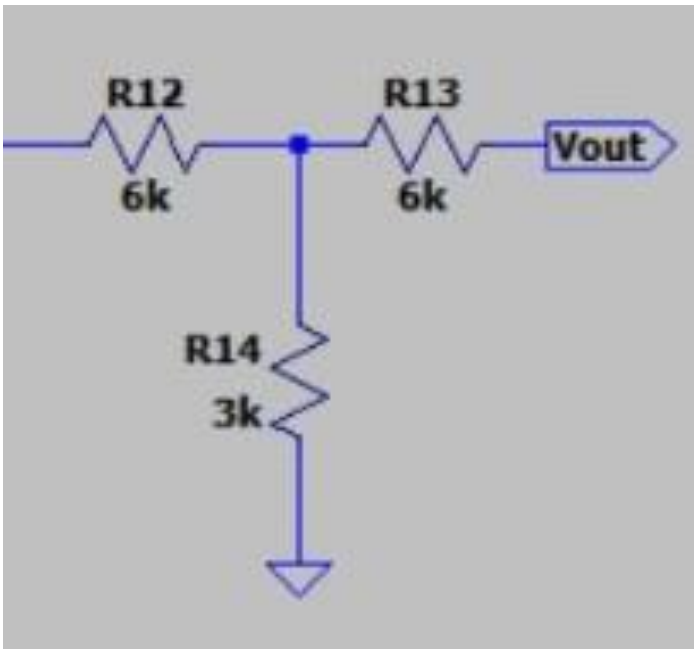


Group no: 2.3

The last version of the circuit is :

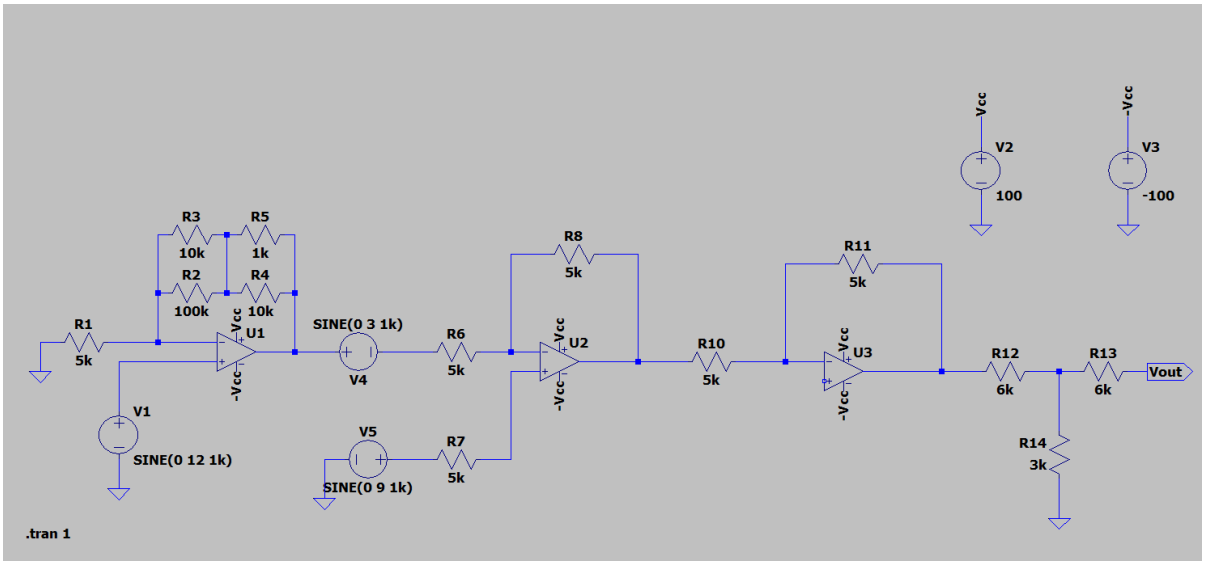


Group no: 2.3


The Output of the circuit is (V_{out}) :

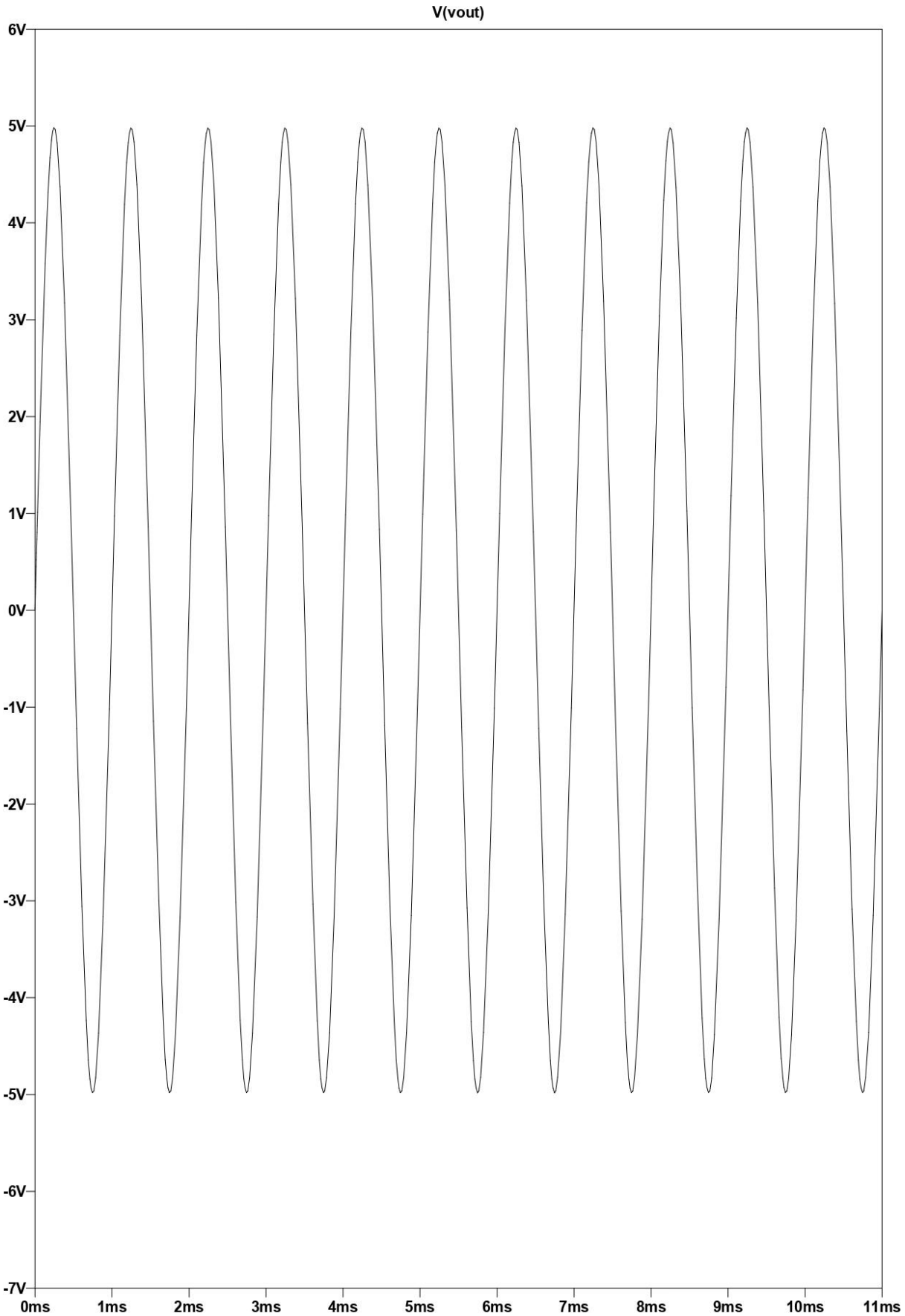

Group no: 2.3

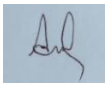Group Member 1: Abdussamed Şahin,150718017, Analyze and draw circuit in ltspice, testing of circuit 

Group Member 2: Mehmet Ali Kamalak,150720062, Calculations and preparing lab report 

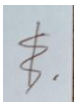Group Member 3: Hüseyin Aydın Tokhan, 150719661,Preparing lab report and analyze 

Group Member 4: Atakan Eroğlu, 150720827, Analyze and solve circuit questions 